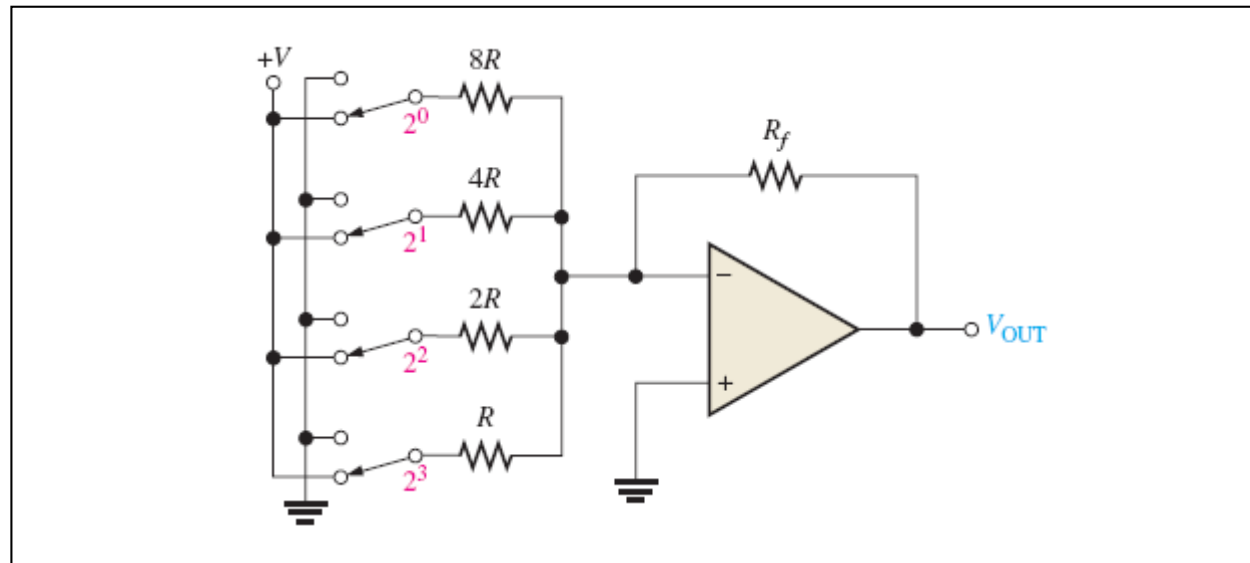




# Ch. 13

## Basic OP-AMP Circuits


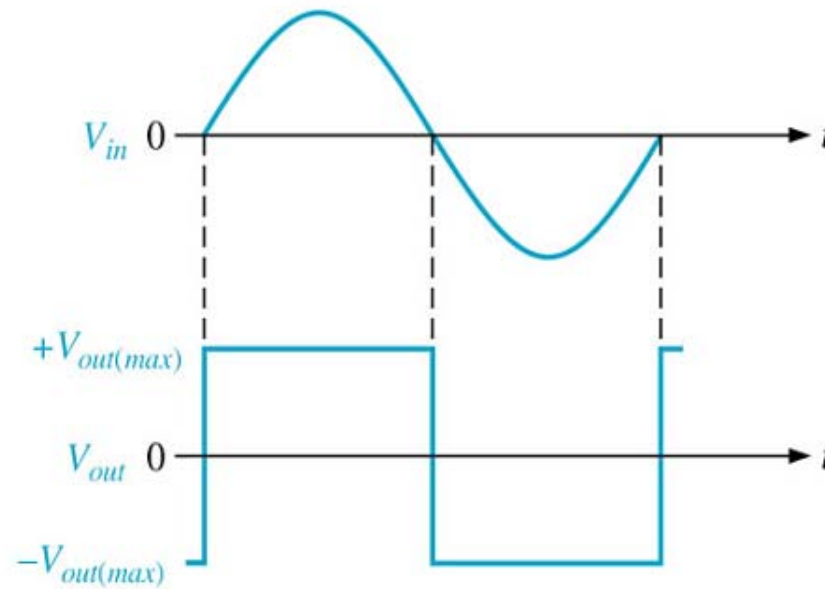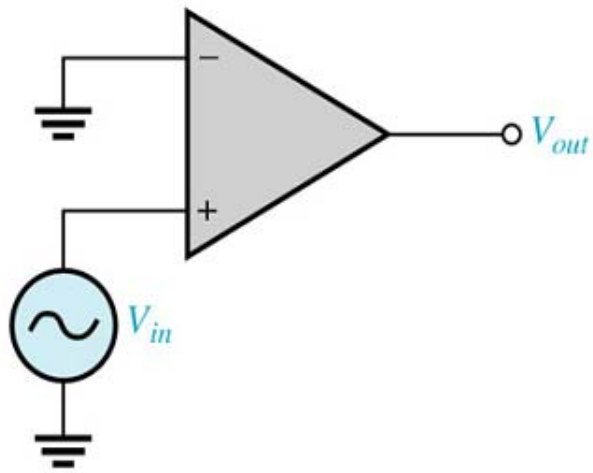
# 비교기(Comparator)


- ☀ 하나의 전압을 다른 전압 (기준 전압, reference)와 비교하기 위한 비선형 장치
- ☀ 영전위 검출




$$\left[ \begin{array}{l} V_{in} > \text{기준 전압} \rightarrow V_{out} = V_{out(max)} \\ V_{in} < \text{기준 전압} \rightarrow V_{out} = V_{out(min)} \end{array} \right.$$

## 영이 아닌 전위 검출



### 기존 배터리

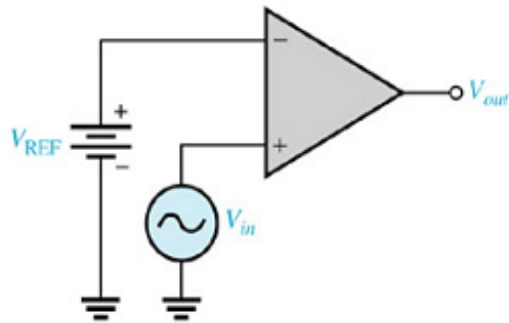

### 기존전압 제너다이오드

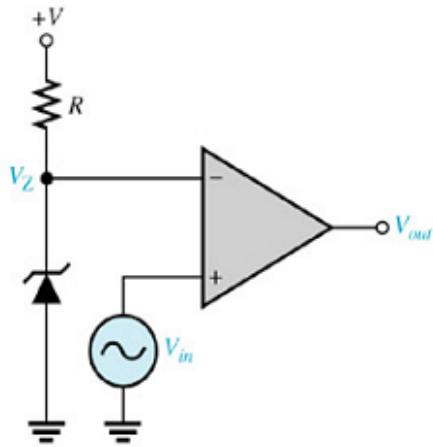



## 기존전압 분배기

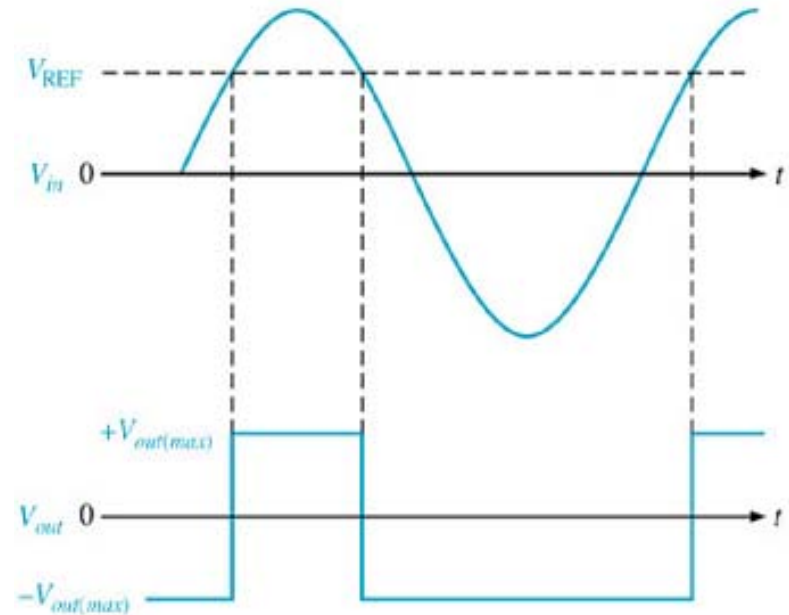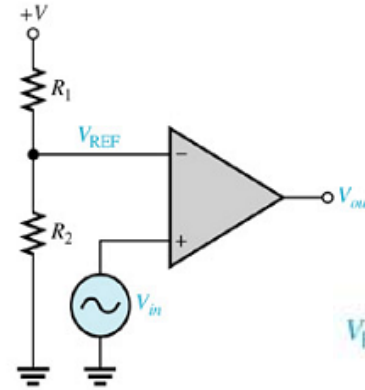

# 비교기

Yun SeopYu

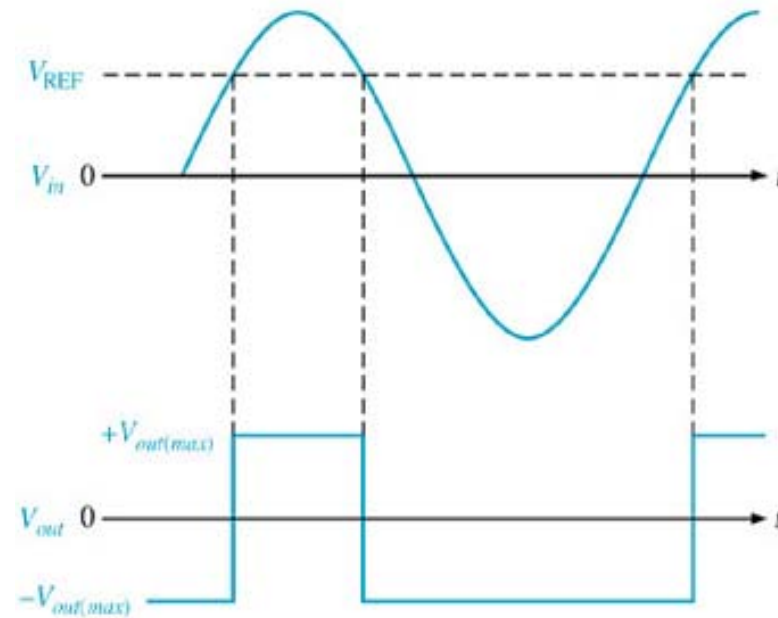
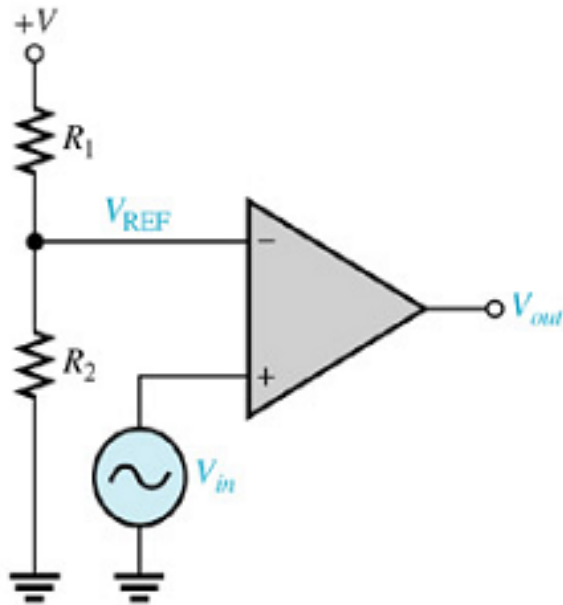
- 예제 13-1:  $V_{out(max)} = 12\text{ V}$ ,  $R_1 = 8.2\text{ k}\Omega$ ,  $R_2 = 1\text{ k}\Omega$



$$V_{REF} = \frac{R_2}{R_1 + R_2} V_{DD} = \frac{1\text{k}}{8.2\text{k} + 1\text{k}} (15) = 1.63\text{V}$$

# 비교기


- 비교기에서 입력 잡음 영향
  - ▣ 입력 잡음 → 출력 에러

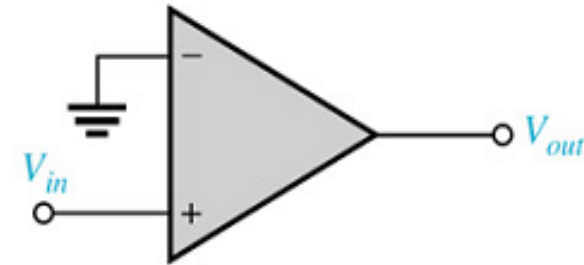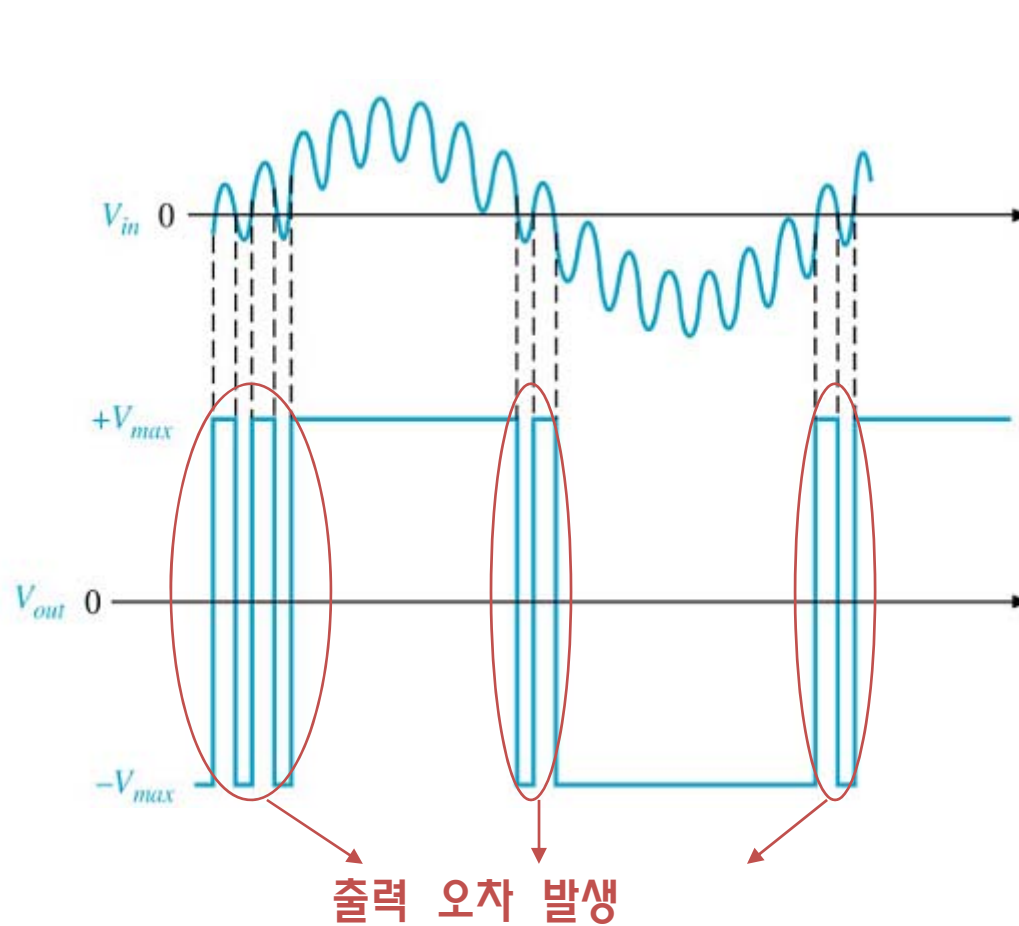

❁ 히스테리시스(hysteresis)에 의한 잡음 영향 줄이기

❁ 잡음 영향:  $\left\{ \begin{array}{l} (+) \rightarrow (-) \\ (-) \rightarrow (+) \end{array} \right\}$  기준 전압 교차시 발생

➔ 히스테리시스 정귀환 이용: 잡음 영향 최소화

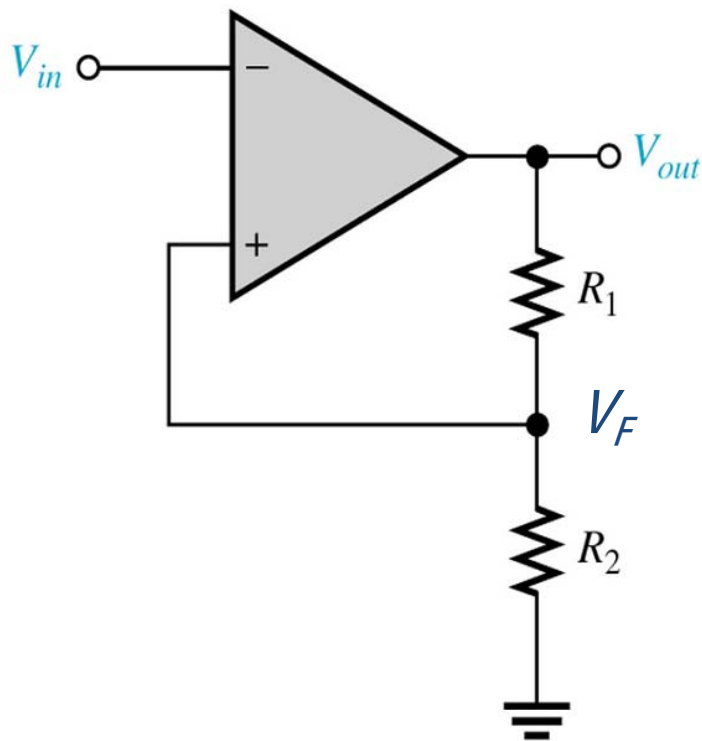

1.  $V_{out} = + V_{out(max)}$   
 $\rightarrow V_F = V_{UTP}$  라 하자

$$V_{UTP} = \frac{R_2}{R_1 + R_2} V_{out(max)}$$

2.  $V_{out} = - V_{out(max)}$   
 $\rightarrow V_F = V_{LTP}$  라 하자

$$V_{LTP} = \frac{R_2}{R_1 + R_2} [-V_{out(max)}]$$



# 비교기

## 히스테리시스에 의한 잡음 영향 줄이기

Case 1)  $V_{in} > V_{UTP}$  (단,  $V_{out} = +V_{out(max)}$ 에서)

- $V_F - V_{in} = V_{UTP} - V_{in} < 0$



$\rightarrow V_{out} = -V_{out(max)}$

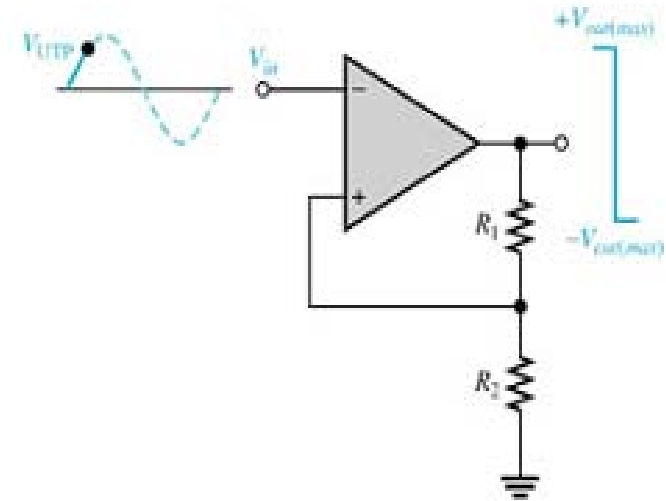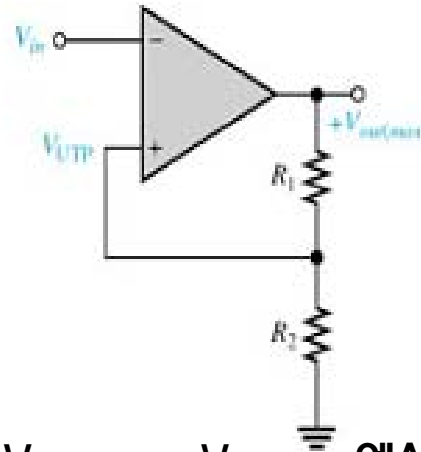



Case 2)  $V_{in} < V_{LTP}$  (단,  $V_{out} = -V_{out(max)}$ 에서)

- $V_F - V_{in} = V_{LTP} - V_{in} > 0$

$\rightarrow V_{out} = +V_{out(max)}$

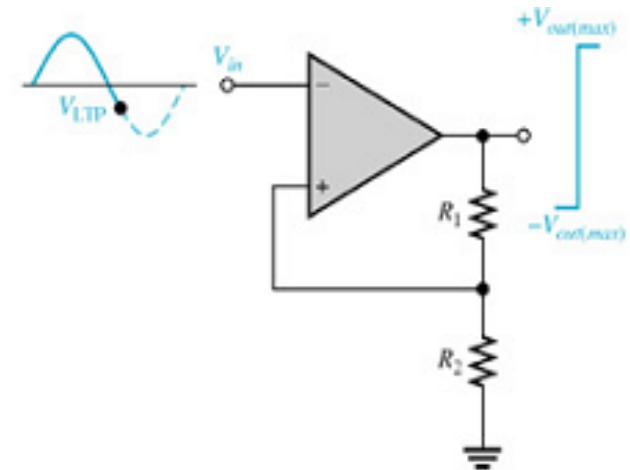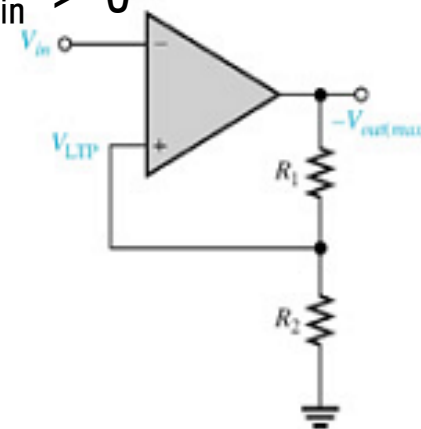

## ❁ 히스테리시스에 의한 잡음 영향 줄이기

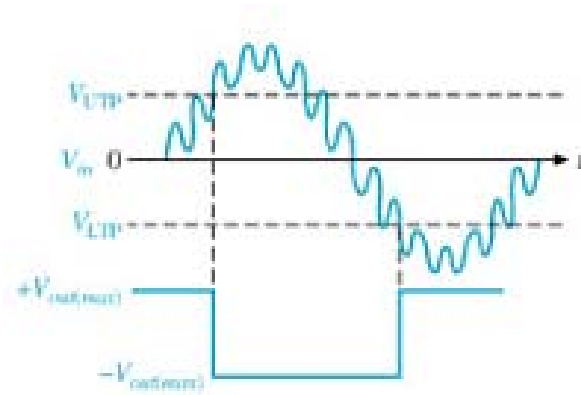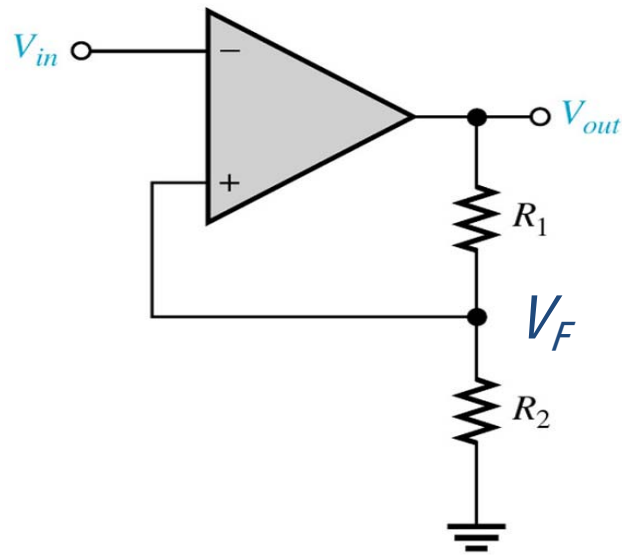

- 잡음 영향이 매우 적음
- 슈미트 트리거 (Schmitt trigger)


$$V_{HYS} = V_{UTP} - V_{LTP}$$

(히스테리시스 전압)



# 비교기

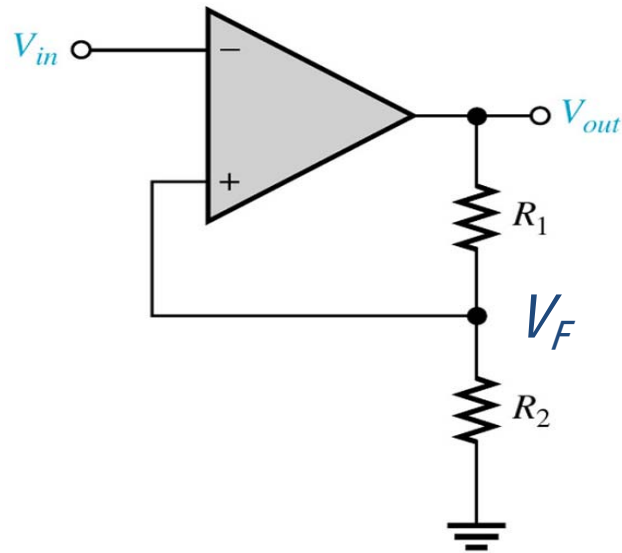- 예제 13-2:  $V_{out(max)} = 5\text{ V}$ ,  $R_1 = 100\text{ k}\Omega$ ,  $R_2 = 100\text{ k}\Omega \rightarrow V_{UTP}$ ,  $V_{LTP}$ ?





$$V_{UTP} = \frac{R_2}{R_1 + R_2} V_{out(max)} = \frac{100\text{k}}{100\text{k} + 100\text{k}} (5) = 2.5\text{V}$$

$$V_{LTP} = \frac{R_2}{R_1 + R_2} [-V_{out(max)}] = \frac{100\text{k}}{100\text{k} + 100\text{k}} (-5) = -2.5\text{V}$$

## 출력 제한 (bounding)



$V_{out} < V_{out(max)}$  로 제한하고자 할 때

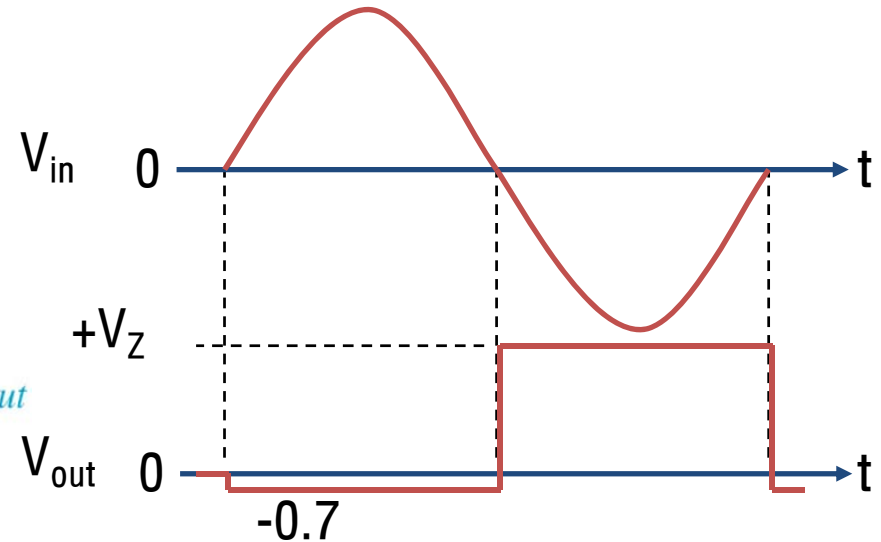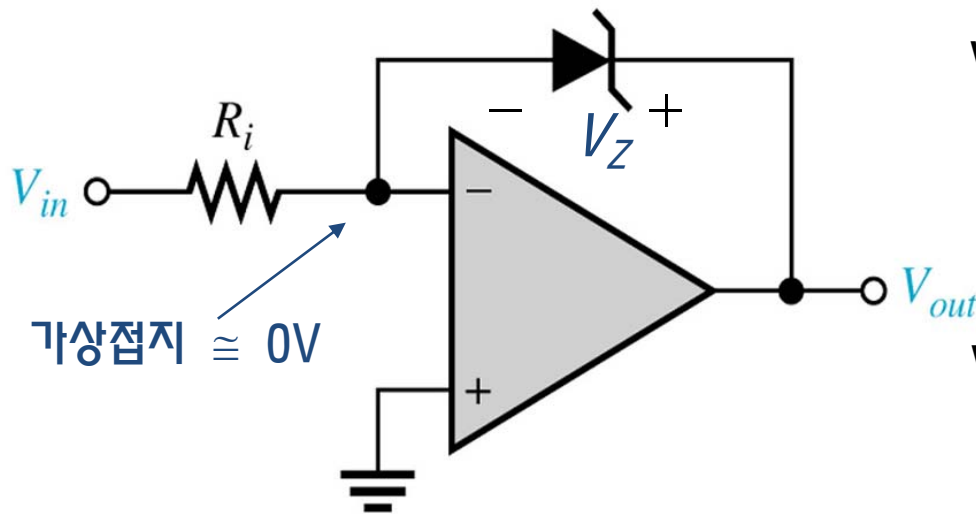

- $V_{out} < -0.7V \rightarrow V_{out} = -0.7V$  (다이오드 전압)
- $-0.7V < V_{out} < V_Z \rightarrow V_{out} = V_{out}$
- $V_{out} > V_Z \rightarrow V_{out} = V_Z$  (제한)

## 출력 제한 (bounding)



$V_{out} < V_{out(max)}$  로 제한하고자 할 때

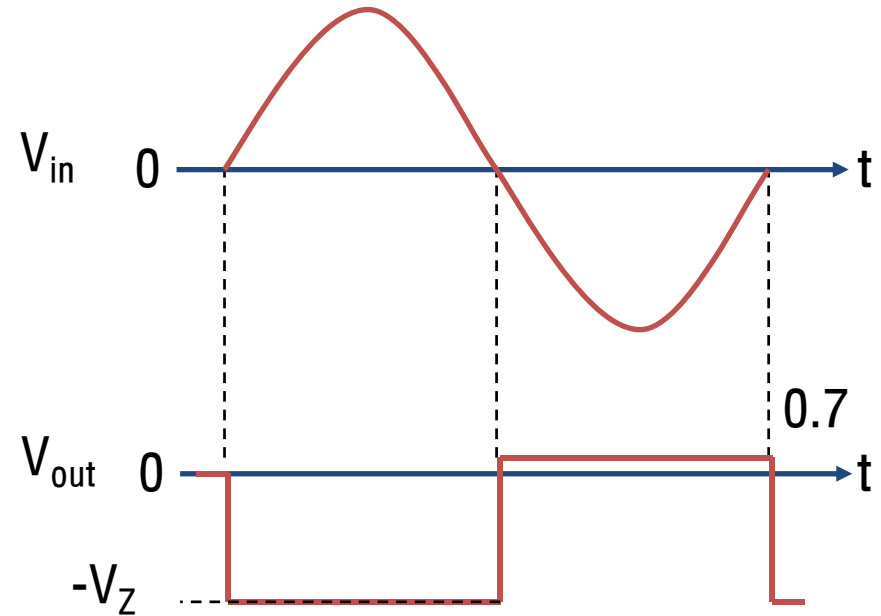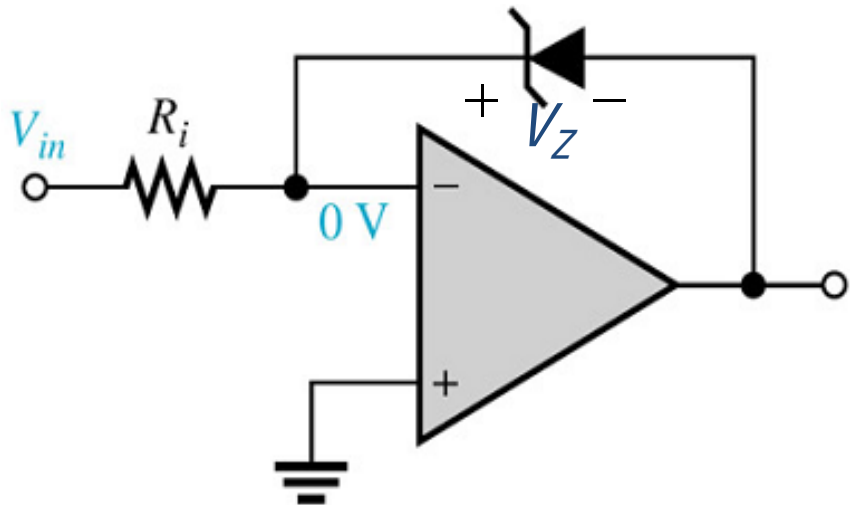



- $V_{out} < -V_Z \rightarrow V_{out} = -V_Z$  (제한)
- $-V_Z < V_{out} < 0.7V \rightarrow V_{out} = V_{out}$
- $V_{out} > 0.7V \rightarrow V_{out} = 0.7V$  (다이오드 전압)

# 비교기

## 출력 제한 (bounding)

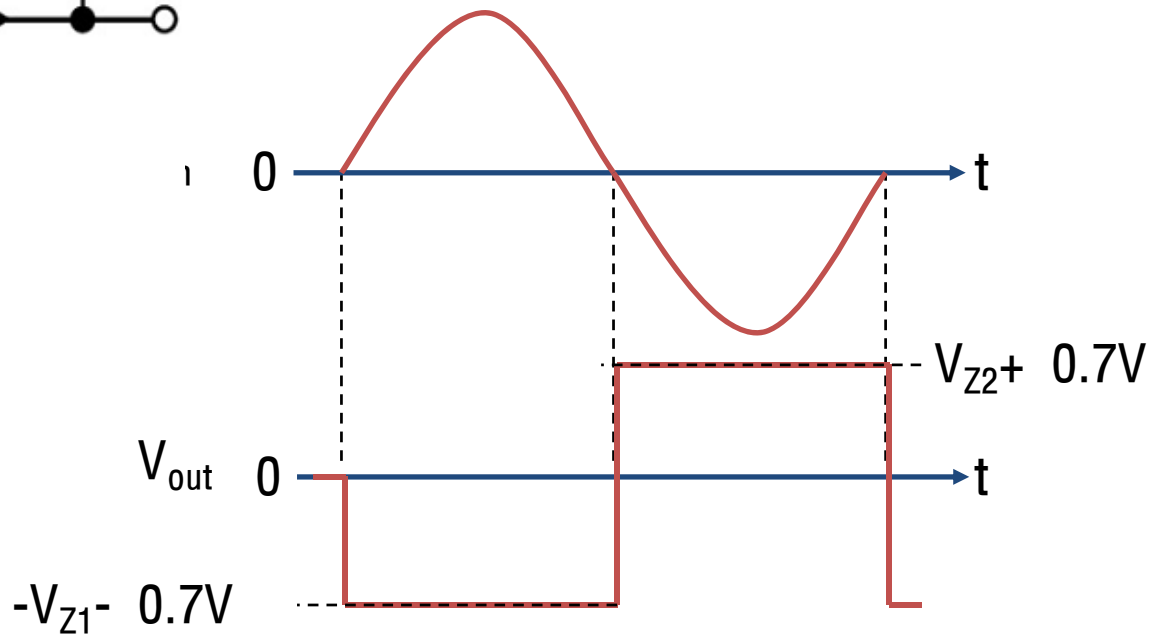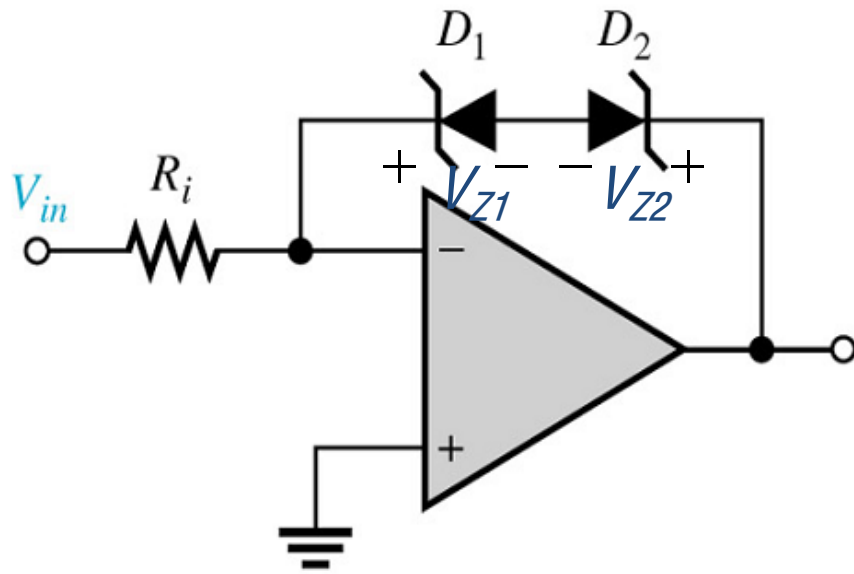

## 예제 13-3: 히스테리시스 + 제너제한

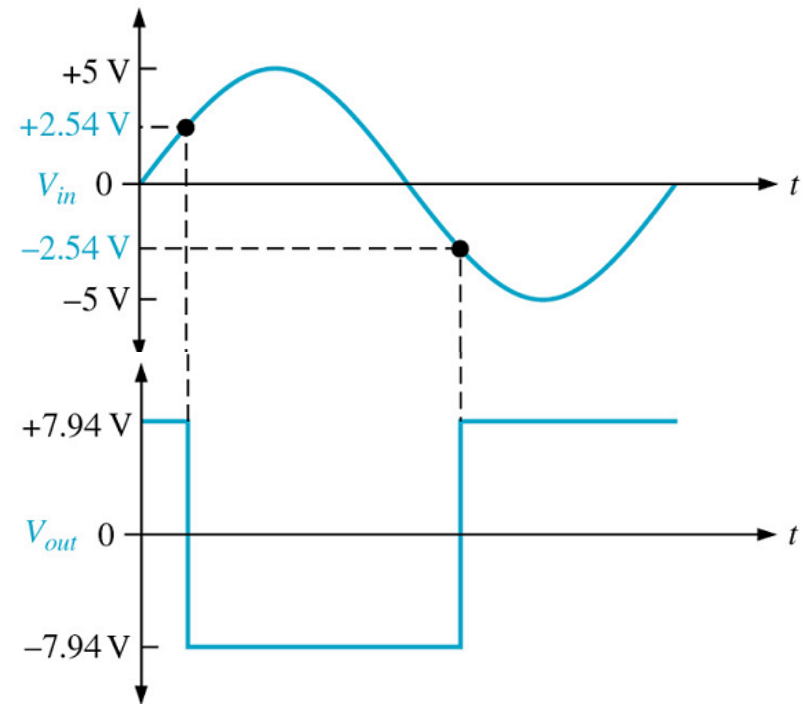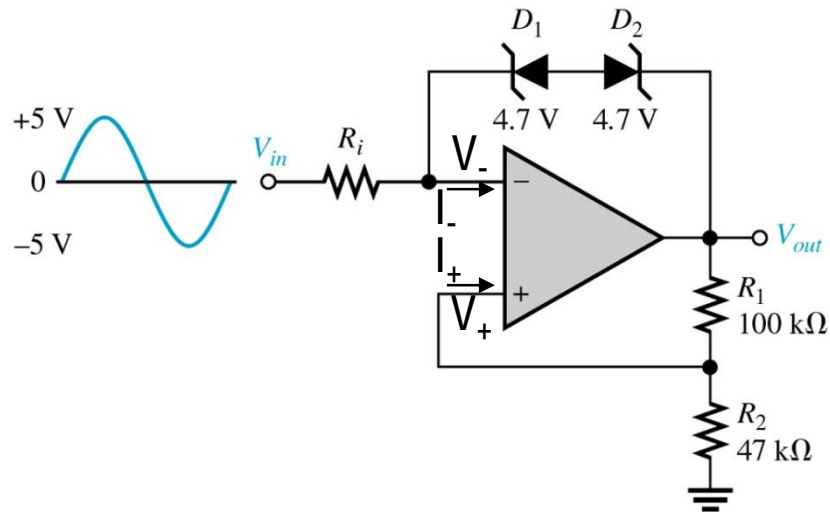

$$I_- \approx I_+ \approx 0 \text{ 이므로 } V_- = V_{out} \pm (4.7 + 0.7) = V_{out} \pm 5.4$$

$$(V_+ - V_-) \text{를 무시하면} \rightarrow V_+ = V_- = V_{out} \pm 5.4$$


$$I_{R2} = I_{R1} = \frac{V_{R1}}{R_1} = \frac{V_{out} - V_+}{100k} = \frac{V_{out} - V_-}{100k} = \frac{V_{out} - V_-}{100k} = \frac{\pm 5.4}{100k} = \pm 54 \mu A$$

$$V_+ = V_{R2} = R_2 I_{R2} = (47k)(\pm 54 \mu) = \pm 2.54 V \longrightarrow V_{UTP} = 2.54 V, V_{LTP} = -2.54 V$$


$$V_{out} = V_{R1} + V_{R2} = \pm(5.4 + 2.54) = \pm 7.94 V$$

# 비교기

## 원도우 비교기

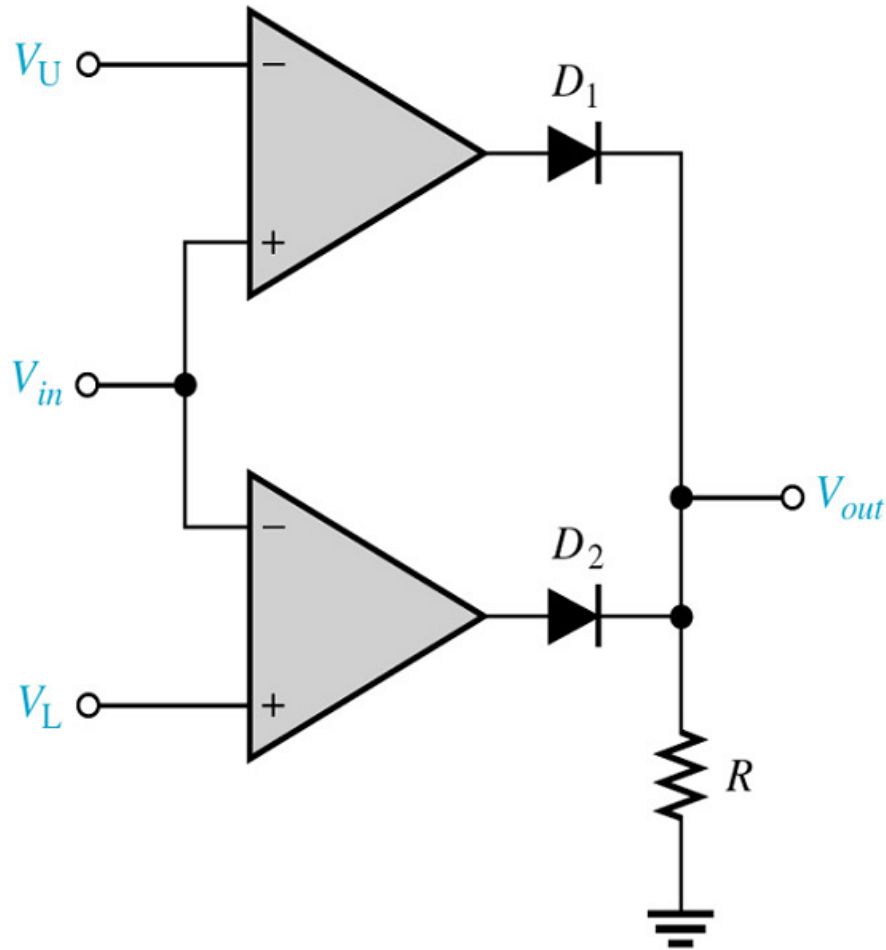

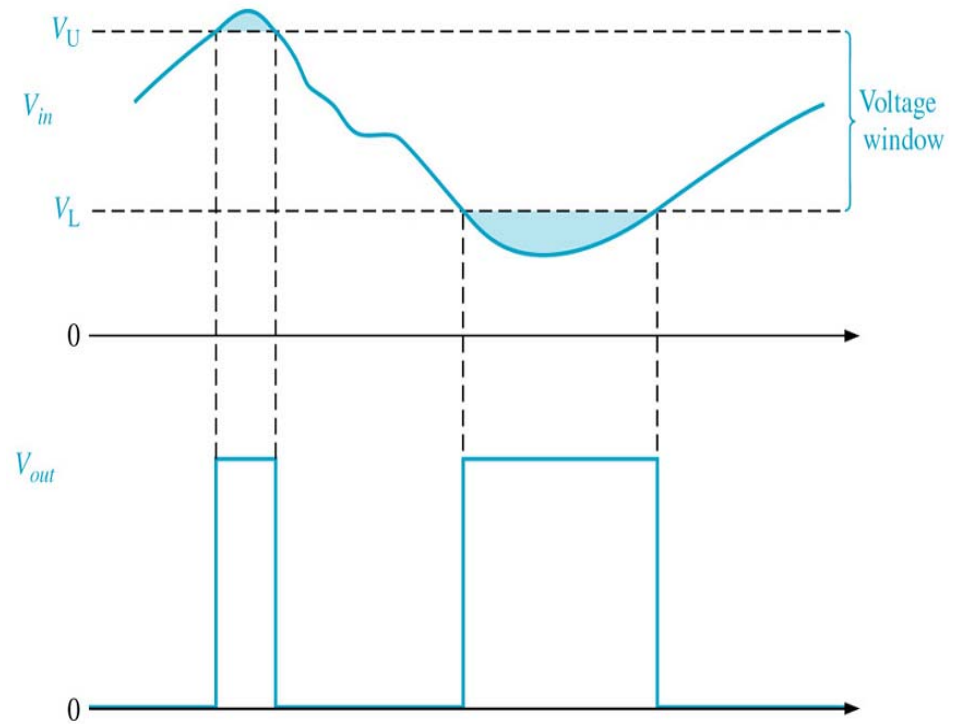
$$V_L < V_{in} < V_U \rightarrow V_{out} = 0$$



## 과열 감출회로(Over-Temperature Sensing Circuit)

❏ 휘스톤 브릿지 회로 이용

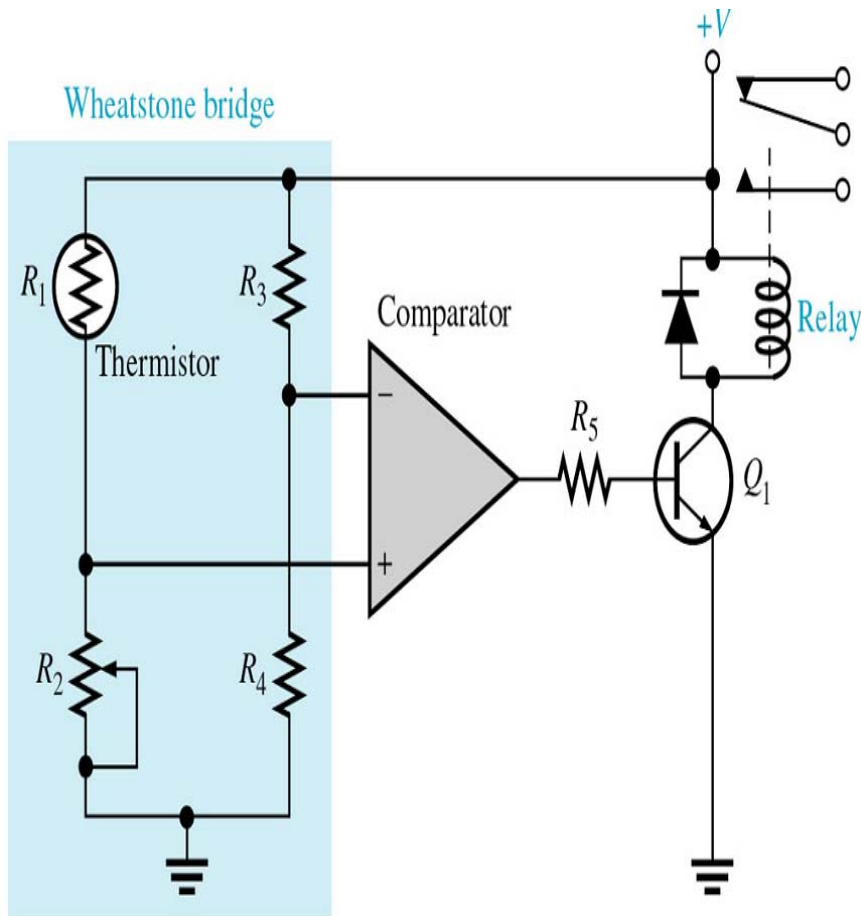

- Thermistor ( $R_1$ ): 부정 온도계수  
(온도  $\uparrow \rightarrow$  저항  $\downarrow$ )
- 가변저항 ( $R_2$ ): 임계온도에서 thermistor  
저항과 같은 값
- 상온 (< 임계온도):  $R_1 > R_2$   
 $\rightarrow V_+$  (상온) <  $V_+$  (임계온도)  
 $\rightarrow V_+$  (상온) <  $V_- \rightarrow V_{out} < 0$   
 $\rightarrow Q_1$  off  
 (단,  $R_3 = R_4 \rightarrow V_- = V_+$  (임계온도))
- 온도  $\uparrow \approx$  임계온도:  $R_1 \approx R_2$   
 $\rightarrow V_+$  (상온)  $\approx V_+$  (임계온도)  
 $\rightarrow V_+$  (상온)  $\approx V_- \rightarrow V_{out} > 0$   
 $\rightarrow Q_1$  동작  $\rightarrow$  Relay 동작

## ⊕ Analog-to-Digital (A/D) 변환

⊕ 예) Simultaneous (or flash) A/D 변환 (전압 분배 방식)

- n자리 → 2진수

  - $2^n - 1$  개 비교기 필요

- 만약 3 자리 →  $V_7 > V_6 > V_5 > \dots > V_2 > V_1$

  - 예  $V_{in} = 3.7 V$ ,  $V_{REF} = 8V$

    - $V_{in} > V_3, V_2, V_1$



    - (1), (2), (3) : “1” , 나머지: “0”

    - 출력:  $D_2D_1D_0 = 011 \rightarrow 3$



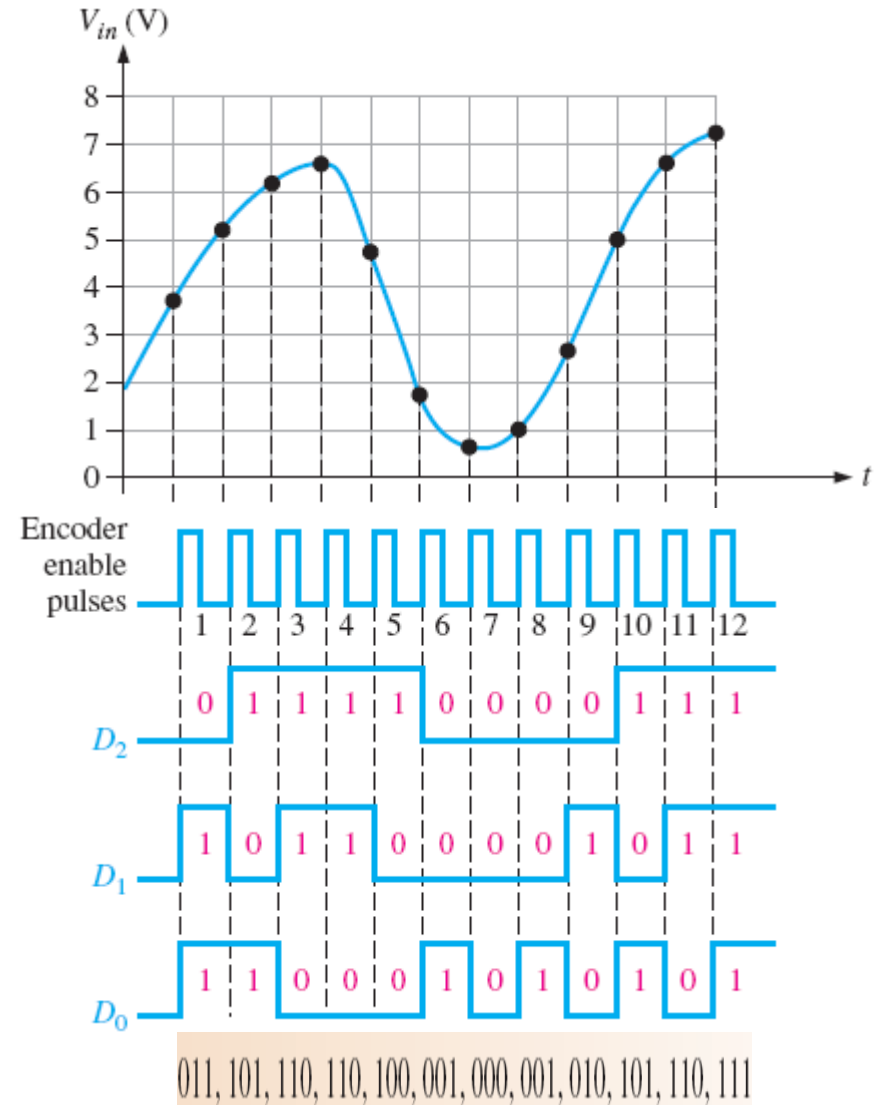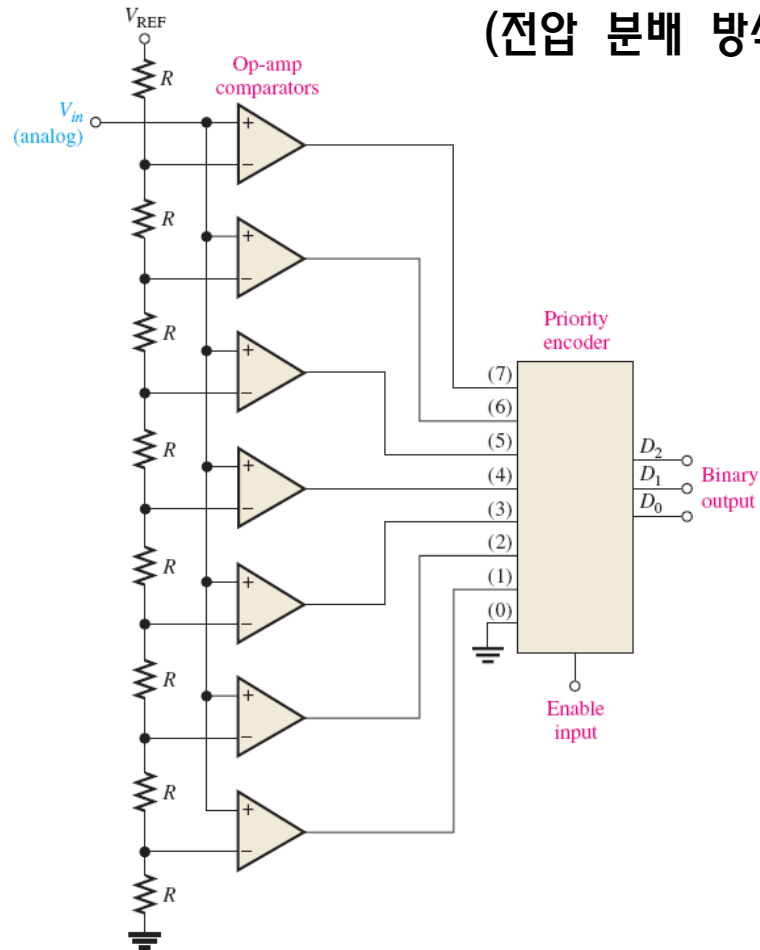
## ⊕ A/D 변환

☒ 예) Simultaneous (or flash) A/D 변환  
(전압 분배 방식)



# 가산기(Summing Amplifier)

## ⊕ n 입력 가산기

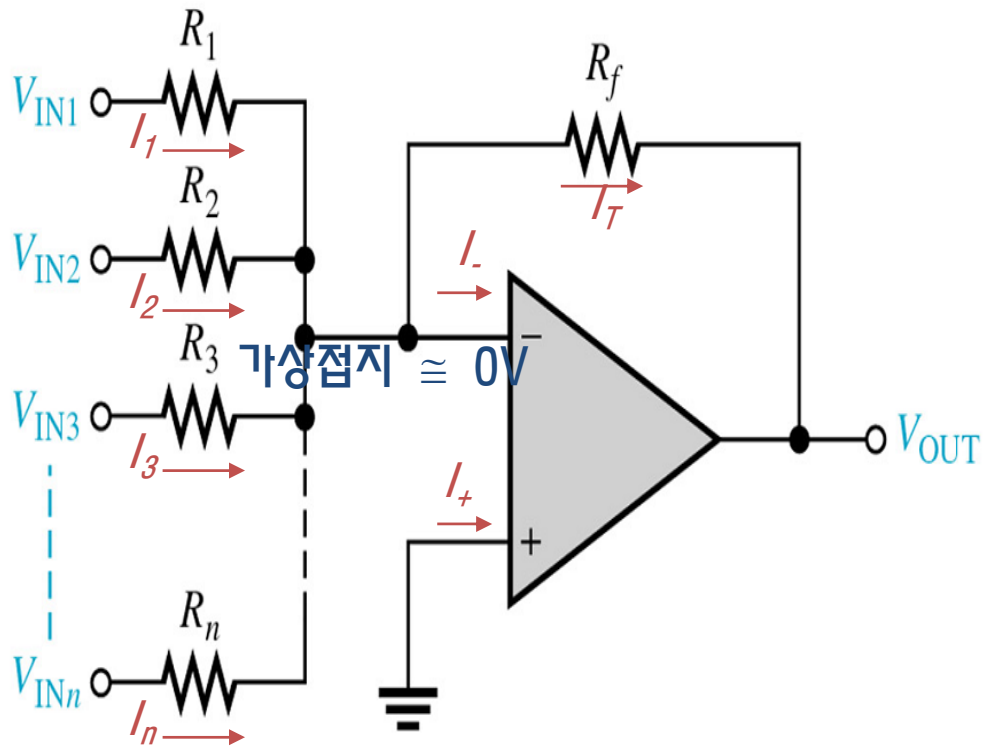

$$I_+ = I_- = 0$$

$$V_+ = V_- = 0 \text{ V (가상접지)}$$

$$I_T = I_1 + I_2 + \dots + I_n$$

$$V_{out} = -I_T R_f$$

$$= -(I_1 + I_2 + \dots + I_n) R_f$$

$$= -(V_{IN1}/R_1 + \dots + V_{INn}/R_n) R_f$$

if  $R_1 = R_2 = \dots = R_n = R_f$

$$\rightarrow V_{out} = -(V_{IN1} + V_{IN2} + \dots + V_{INn})$$

- 1보다 큰 이득을 갖는 가산기

- $R_1 = R_2 = \dots = R_n = R$

$$V_{out} = -\frac{R_f}{R} (V_{in1} + V_{in2} + \dots + V_{inN})$$

- 평균 증폭기

- $R_f/R = 1/n$

$$V_{out} = -\frac{V_{in1} + V_{in2} + \dots + V_{inN}}{n}$$


- 스케일링 가산기

$$V_{out} = -\left(\frac{R_f}{R_1} V_{in1} + \frac{R_f}{R_2} V_{in2} + \dots + \frac{R_f}{R_n} V_{inN}\right)$$

- 입력전압 1의 가중치:  $R = R_f$
  - 입력전압 2의 가중치:  $R = 2R_f$

# 가산기

## 스케일링 가산기 응용



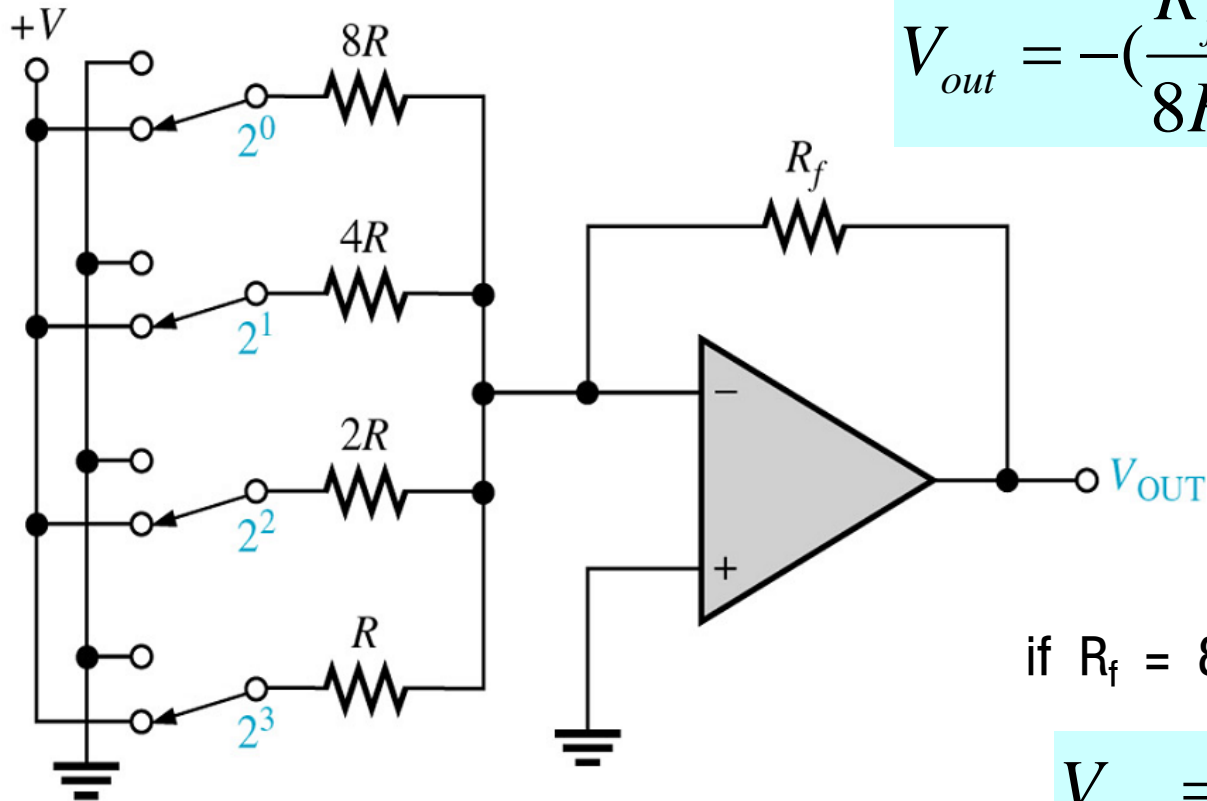


$$V_{out} = -\left(\frac{R_f}{8R} + \frac{R_f}{4R} + \frac{R_f}{2R} + \frac{R_f}{R}\right)V$$

if  $R_f = 8R$

$$V_{out} = -(1 + 2 + 4 + 8)V$$

## 스케일링 가산기 응용 - 예제 13-9

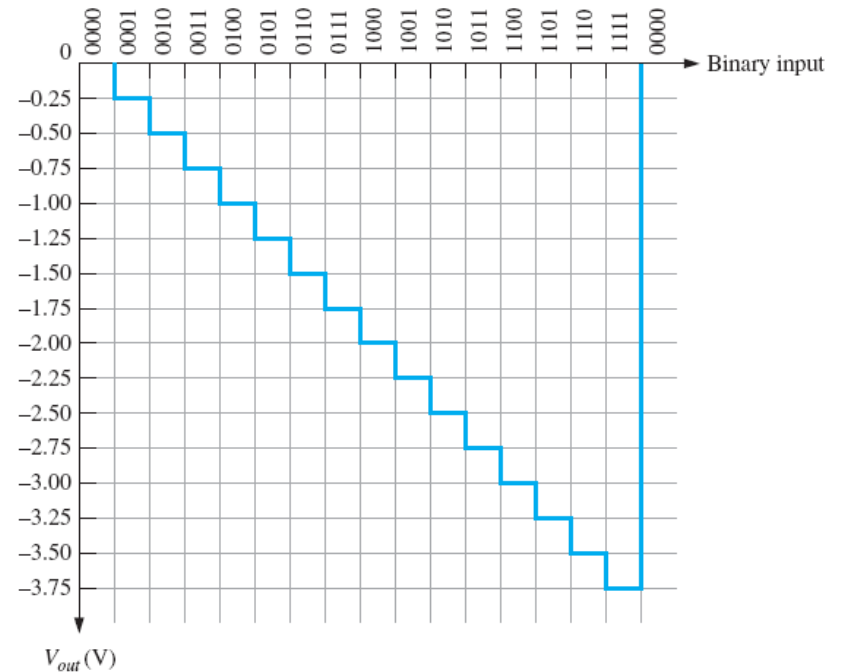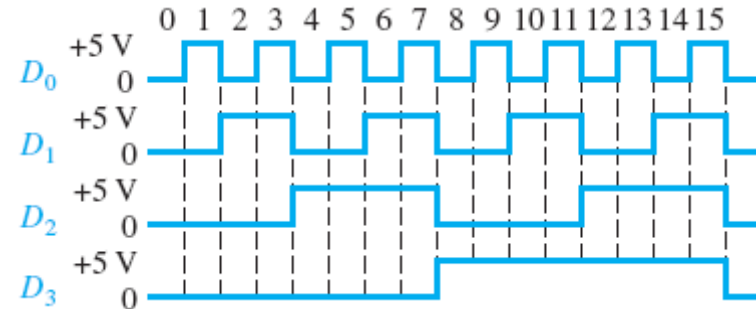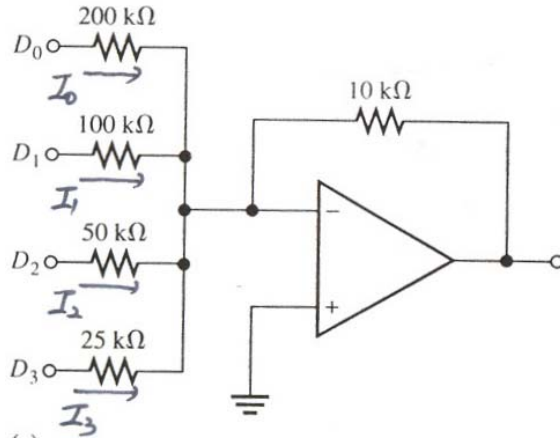

$$I_0 = 5/200k = 0.025mA$$

$$I_1 = 5/100k = 0.05mA$$

$$I_2 = 5/50k = 0.1mA$$

$$I_3 = 5/25k = 0.2mA$$

$$V_{OUT(D0)} = -R_f I_0 = -(10k)(0.025m) = -0.25V$$

$$V_{OUT(D1)} = -R_f I_1 = -(10k)(0.05m) = -0.5V$$

$$V_{OUT(D2)} = -R_f I_2 = -(10k)(0.1m) = -1V$$



$$V_{OUT(D3)} = -R_f I_3 = -(10k)(0.2m) = -2V$$

예)  $D_3D_2D_1D_0 = 0001 = 1 \rightarrow -0.25V$

# 적분기와 미분기
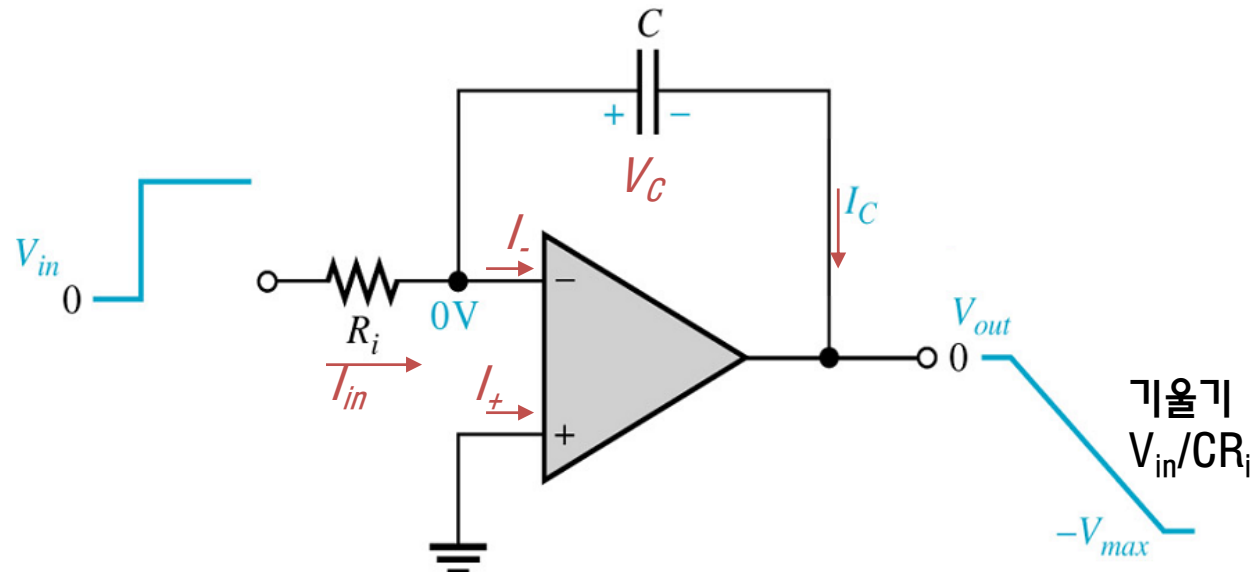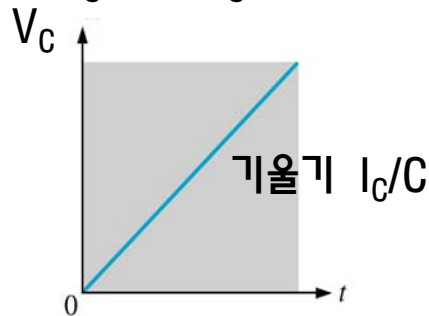
## 적분기 (Integrator)

- 캐패시터 전하  
 $Q = I_C t = C V_C$   
 $V_C = (I_C / C) t$



$$I_+ = I_- = 0, V_+ = V_- = 0 \text{ V (가상접지)}$$

$$I_{in} = V_{in} / R_i = I_C$$

$$V_C = (I_C / C) t = (V_{in} / CR_i) t \rightarrow V_{out} = -V_C$$


$$\rightarrow \Delta V_{out} = -\Delta V_C = (-V_{in} / CR_i) \Delta t$$

$$\frac{\Delta V_{out}}{\Delta t} = -\frac{V_{in}}{CR_i} \rightarrow V_{out} = -\frac{1}{CR_i} \int V_{in} dt$$

# 적분기와 미분기

Yun SeopYu

## 예제 13-10

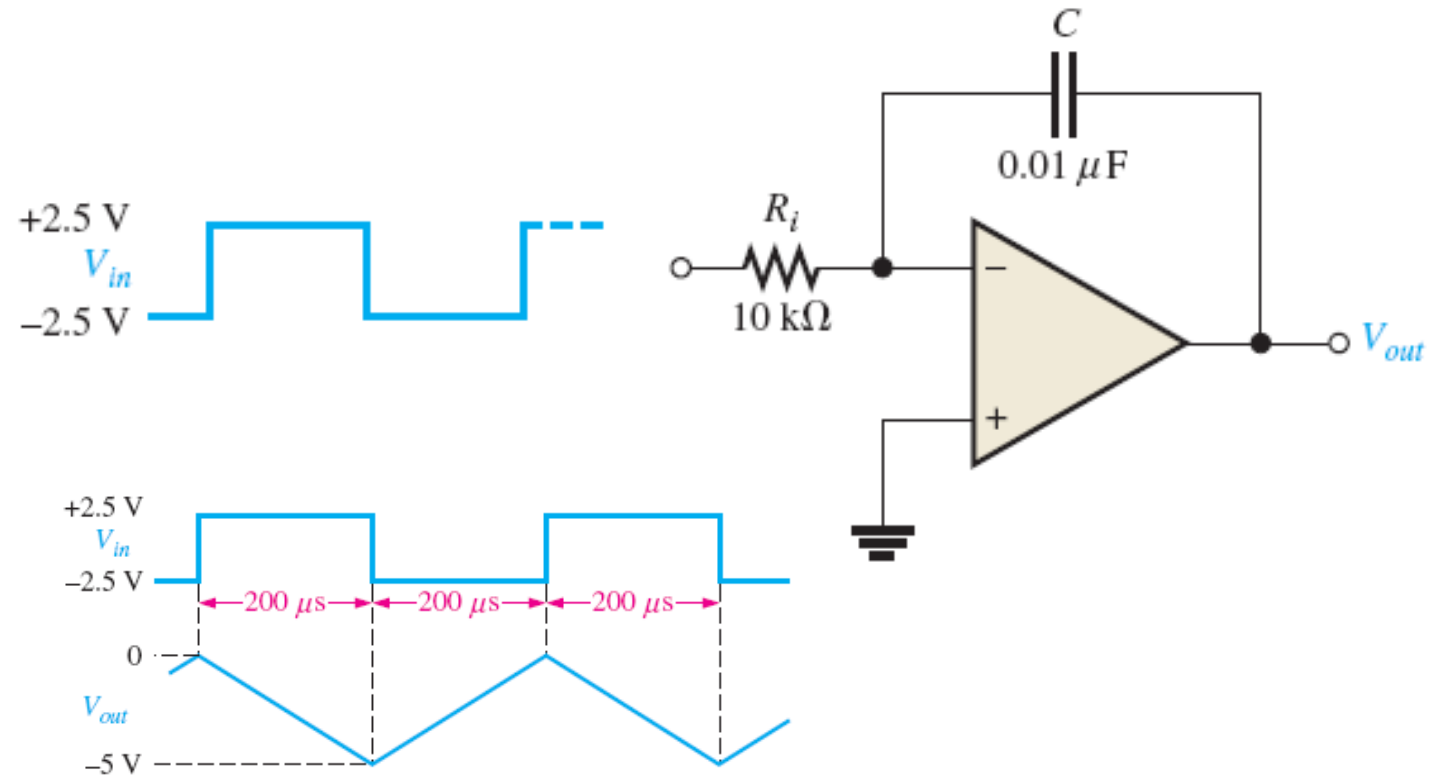


$$\frac{\Delta V_{out}}{\Delta t} = -\frac{V_{in}}{CR_i} = -\frac{2.5}{(0.01\mu)(10\text{k})} = -25\text{kV/s} = -25\text{mV}/\mu\text{s}$$

$$\Delta V_{out} = (25\text{mV}/\mu\text{s})\Delta t = (25\text{mV}/\mu\text{s})(200\mu\text{s}) = 5\text{V}$$

# 적분기와 미분기

## 미분기 (Differentiator)

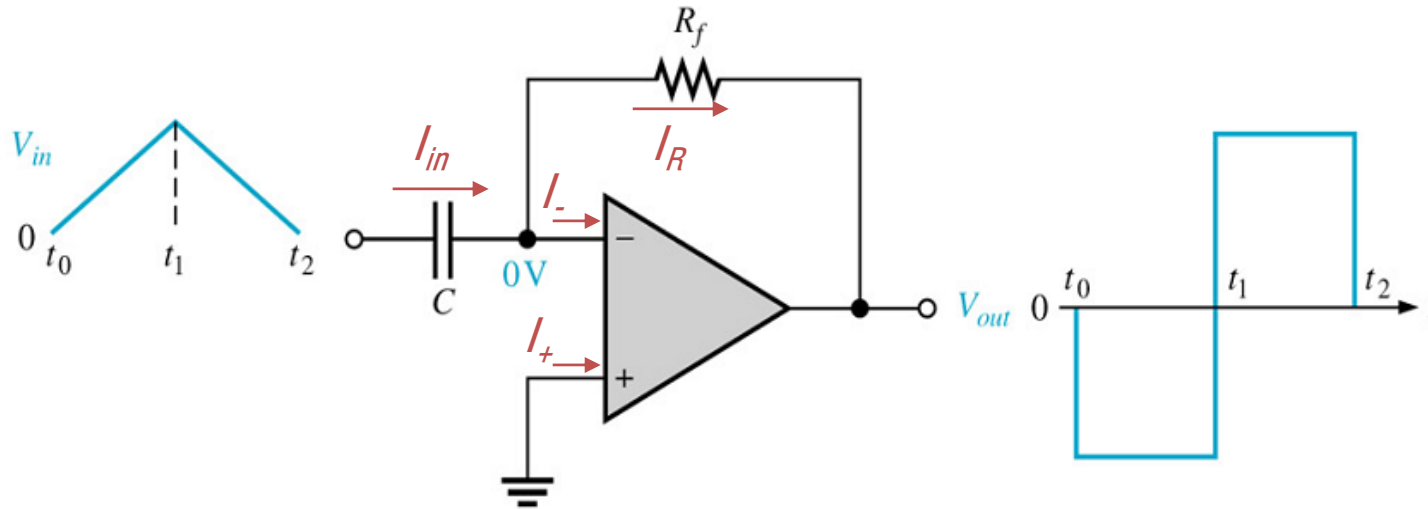

$$I_+ = I_- = 0, V_+ = V_- = 0 \text{ V (가상접지)}$$

$$Q = I_c t = C V_C = C V_{in}$$

$$V_{in} = (I_{in}/C)t$$


$$I_{in} = I_R \rightarrow (C V_{in}/t) = - V_{out}/R_f$$

$$V_{out} = -CR_f \left( \frac{V_{in}}{t} \right) \longrightarrow V_{out} = -CR_f \frac{dV_{in}}{dt}$$



# 적분기와 미분기

## 예제 13-11

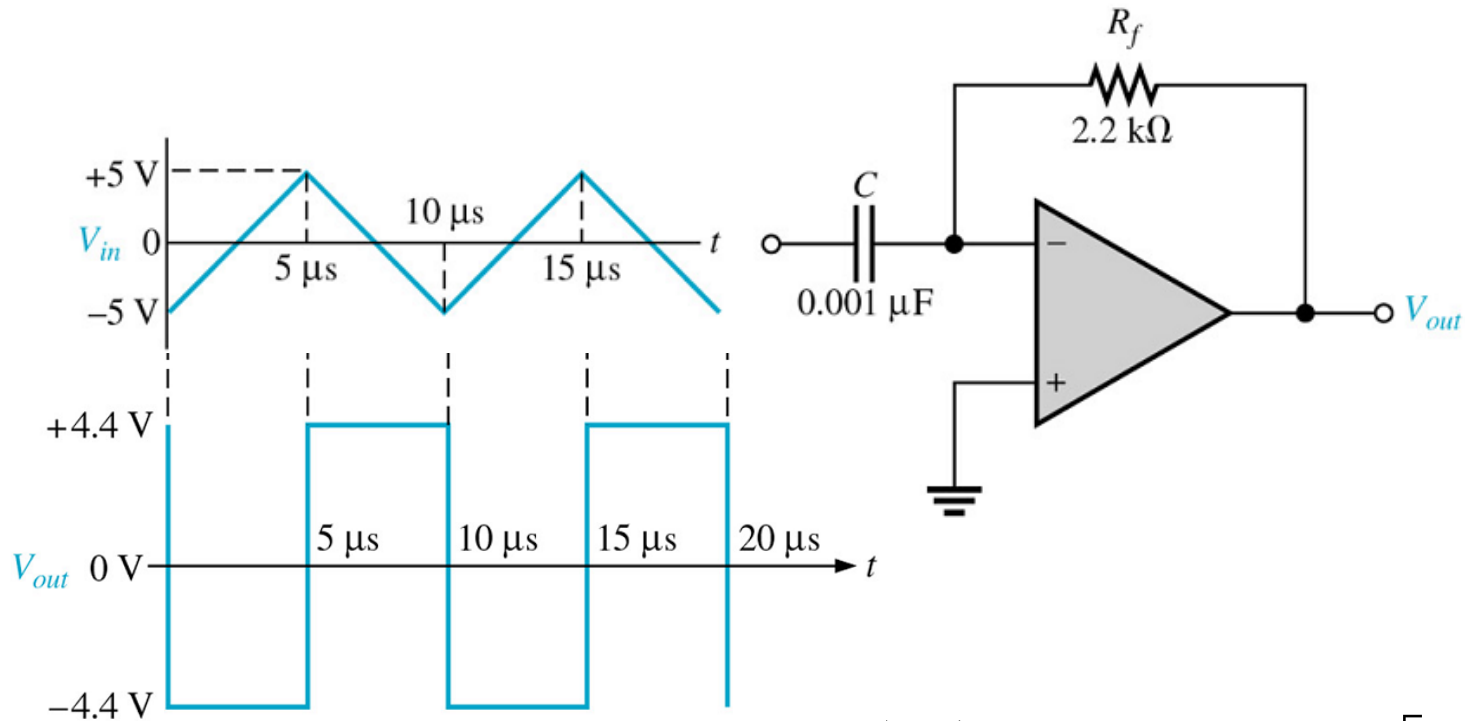


$$V_{out} = -CR_f \left( \frac{V_{in}}{t} \right) = -(0.001 \mu)(2.2 \text{ k}) \left[ \frac{+5 - (-5)}{5 \mu} \right] = -4.4 \text{ V}$$


# 적분기와 미분기

Yun SeopYu

*The Practical Integrator*

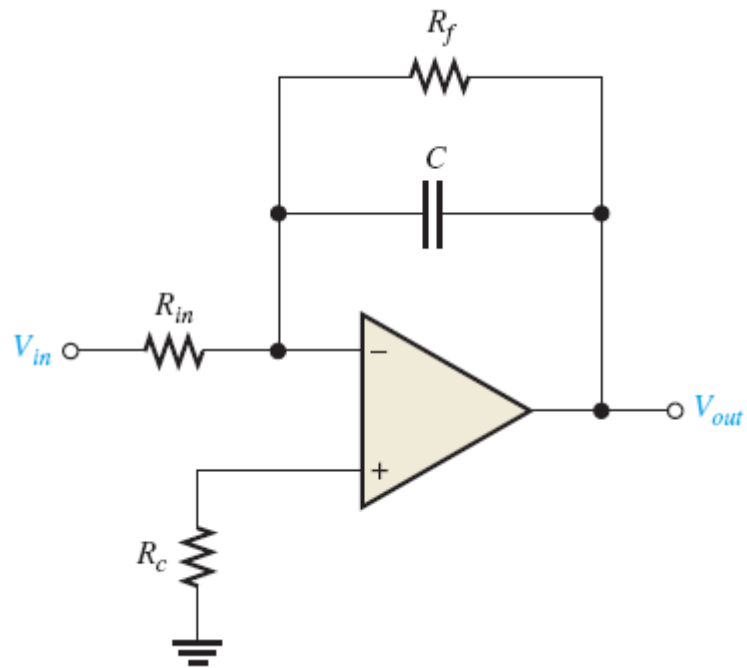


*The Practical Differentiator*

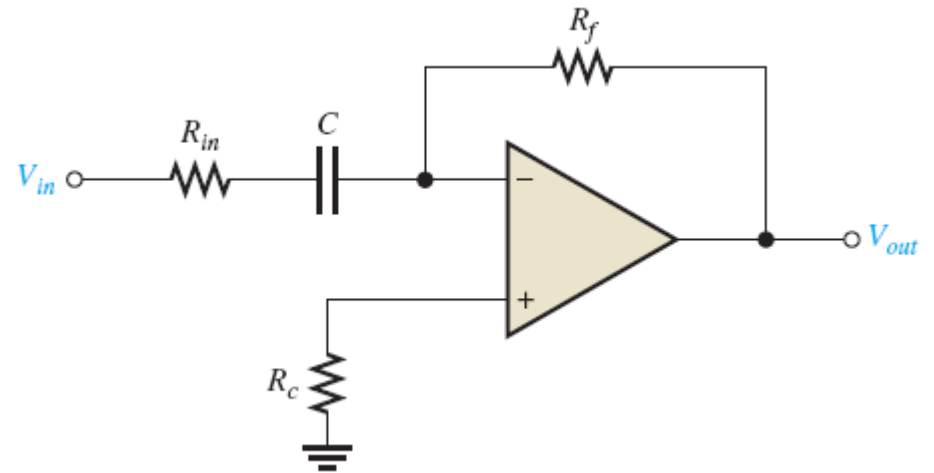



**Homework**  
**All Examples**  
**Selected Problems(P.711-717):**  
**2,3,4,8,10,11,14,16,19**

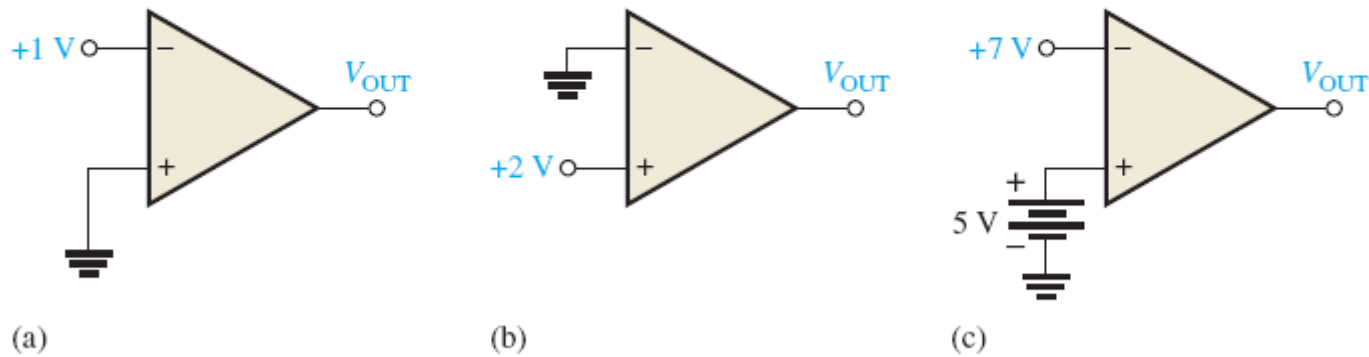
2. Determine the output level (maximum positive or maximum negative) for each comparator in Figure 13–60.



▲ FIGURE 13-60


3. Calculate the  $V_{UTP}$  and  $V_{LTP}$  in Figure 13–61.  $V_{out(max)} = \pm 10\text{ V}$ .  
 4. What is the hysteresis voltage in Figure 13–61?

▶ FIGURE 13-61

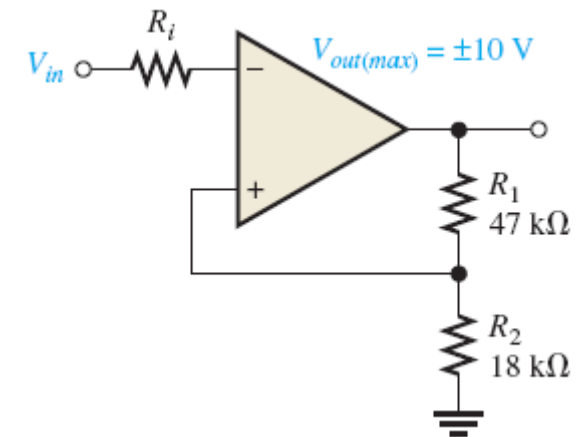


8. Determine the output voltage waveform in Figure 13–64.

▶ FIGURE 13–64

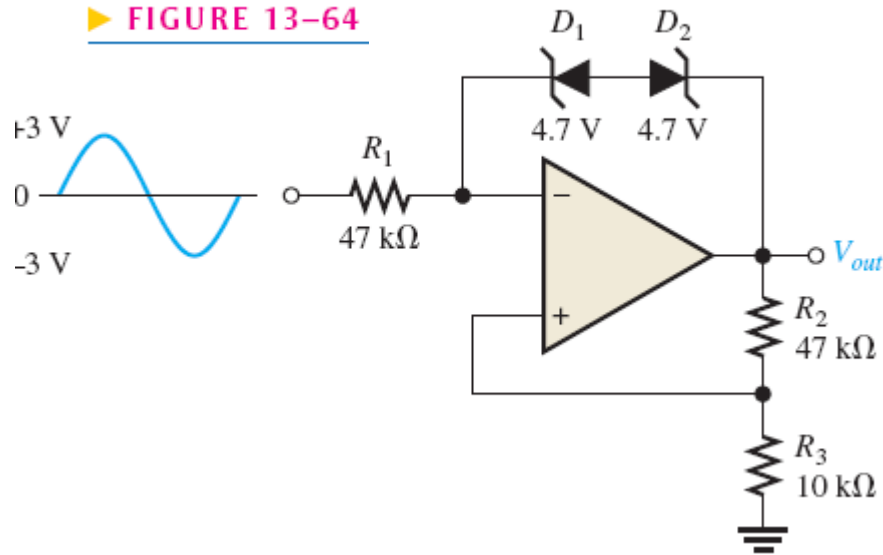

▶ FIGURE 13–66

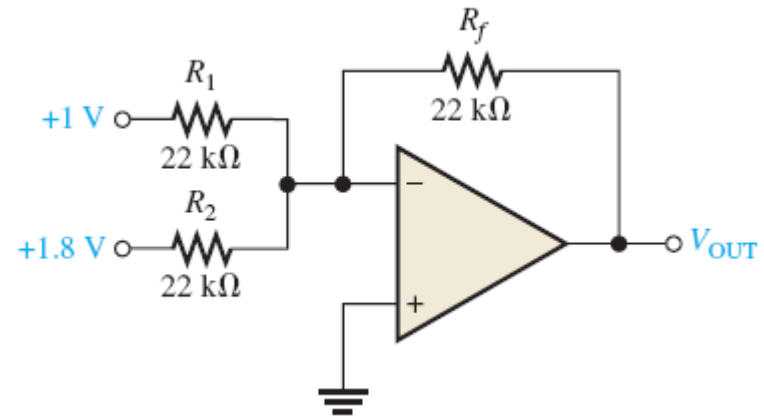


10. Refer to Figure 13–66. Determine the following:

- (a)  $V_{R1}$  and  $V_{R2}$     (b) Current through  $R_f$     (c)  $V_{OUT}$


11. Find the value of  $R_f$  necessary to produce an output that is five times the sum of the inputs in Figure 13–66.

14. Determine the values of the input resistors required in a six-input scaling adder so that the lowest weighted input is 1 and each successive input has a weight twice the previous one.  $V_{ref} = 100 \text{ k}\Omega$ .

▶ FIGURE 13-67

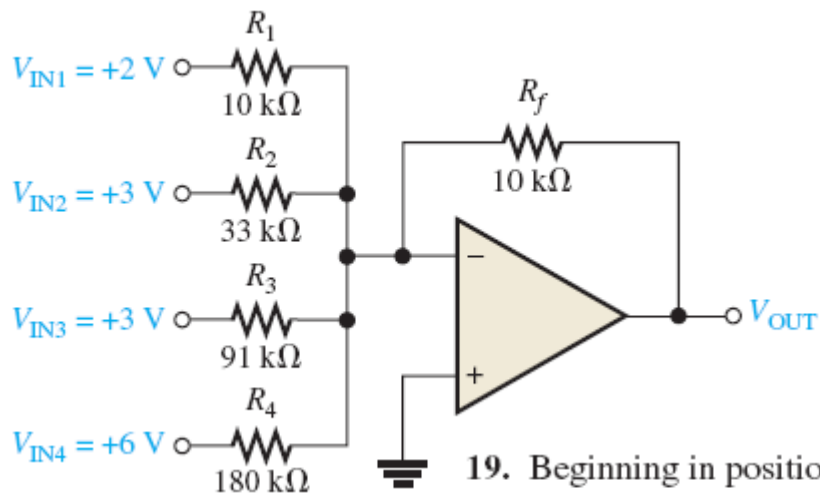

▶ FIGURE 13-70

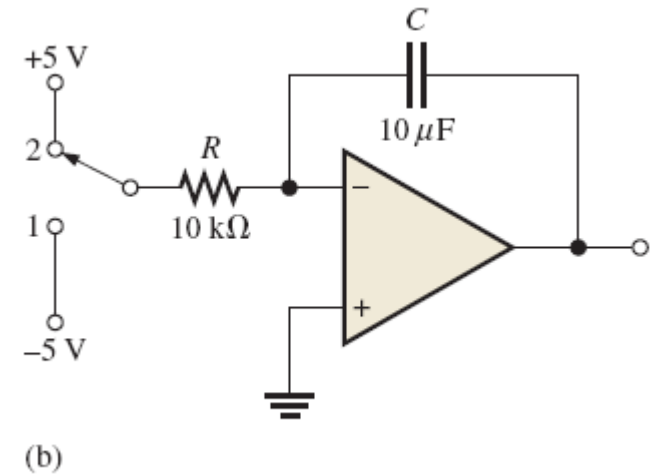

19. Beginning in position 1 in Figure 13-70(b), the switch is thrown into position 2 and held there for 10 ms, then back to position 1 for 10 ms, and so forth. Sketch the resulting output waveform if its initial value is 0 V. The saturated output levels of the op-amp are  $\pm 12 \text{ V}$ .

16. A triangular waveform is applied to the input of the circuit in Figure 13-69 as shown. Determine what the output should be and sketch its waveform in relation to the input.

▶ FIGURE 13-69

